

[20 Q x 0.5 = 10 marks]

1. The current through 5 KΩ resistor is \_\_\_\_\_ mA when the power dissipated by that resistor is 20 mW.

- [a] 2
- [b] 4
- [c] 6
- [d] 8

2. The value of I for the circuit of figure 1 is \_\_\_\_\_ mA

- [a] 1.8
- [b] -1.8
- [c] -3.6
- [d] 3.6

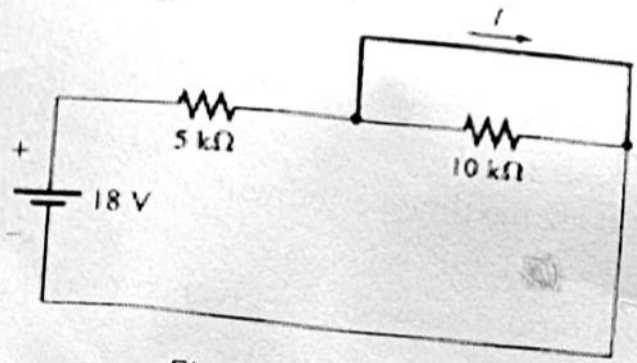


Figure 1

Handwritten notes for question 1:  
 $P = I^2 R$   
 $20 = I^2 \times 5$   
 $I^2 = 4$   
 $I = 2$

Handwritten note for question 2:  
 $I = \frac{V}{R} = \frac{18}{5} = 3.6$

3. For a star network of three equal resistors, the value of each resistor of the equivalent delta network is equal to \_\_\_\_\_ times the value of any resistor of the star network.

- [a] 1/3
- [b] 3
- [c] 1/2
- [d] 2

4. The power mentioned on the name plate of an electric motor indicates \_\_\_\_\_

- [a] the power drawn in KW
- [b] the power drawn in kVA
- [c] the gross power
- [d] the output power at the shaft

5. The power consumed in a circuit element will be least when the phase difference between the current and voltage is \_\_\_\_\_.

- [a] 180°
- [b] 90°
- [c] 60°
- [d] 0°

6. The inductance needed to resonance at 5 kHz with a capacitance of 12 nF is \_\_\_\_\_.

- [a] 2652 H
- [b] 3.333 H
- [c] 11.844 H
- [d] 84.43 mH

7. A 20 W FM radio connected in a car with a 6 V battery is to be moved to a new car with a 12V battery. The value of resistor that should be connected in series with the radio to limit the current is \_\_\_\_\_ Ω.

- [a] 1.8
- [b] 7.2
- [c] 3.6
- [d] 4.2

8. The magnitude of voltage across resistor is \_\_\_\_\_ in the circuit of figure-2.

- [a] 33.33V
- [b] 60V
- [c] 80 V
- [d] 100 V

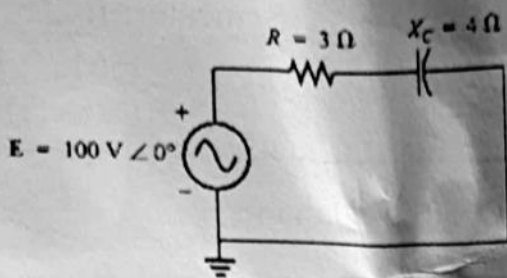


Figure 2

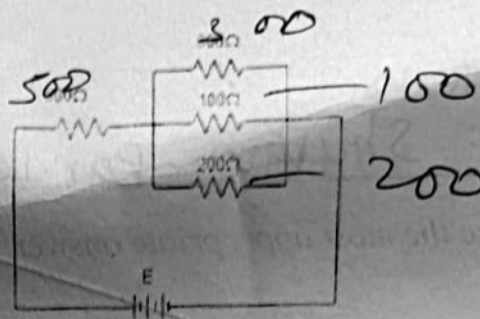


Figure 3

9. For maximum power transfer to the load, the value of load resistance ( $R_L$ ) should be \_\_\_\_\_.
- [a] maximum      [b] minimum      [c]  $R_{TH}$       [d] ~~4~~ $R_{TH}$
10. The current across the short circuit is \_\_\_\_\_.
- [a] zero      [b] negative      [c] maximum      [d] minimum
11. For any value of battery voltage, E in the figure-3 the smallest current will flow in the resistance of \_\_\_\_\_.
- [a] ~~300~~ 300 Ω      [b] 500 Ω      [c] 100 Ω      [d] 200 Ω
12. For a frequency of 200 Hz the time period will be \_\_\_\_\_.
- [a] 0.05 seconds      [b] 0.005 seconds      [c] 0.5 seconds      [d] 0.0005 seconds
13. What is the phase relationship between the given sinusoidal waveforms?  
 $V = 10 \sin(\omega t + 30^\circ)$  and  $I = 5 \sin(\omega t - 70^\circ)$
- [a] V leads I by  $70^\circ$       [b] I leads V by  $30^\circ$       [c] V leads I by  $100^\circ$       [d] I leads V by  $100^\circ$
14. The apparent power drawn by an AC circuit is 10kVA and active power is 8KW. The reactive power in the circuit is \_\_\_\_\_.
- [a] 2 kVAR      [b] 6 kVAR      [c] 8 kVAR      [d] 10 kVAR
15. The peak value of a sine wave is 200 V. The RMS value is \_\_\_\_\_.
- [a] 127.7 V      [b] 200 V      [c] 82.8 V      [d] 141.4 V
16. A series R-L-C circuit has a series resonating frequency of 12,000 Hz. If  $R = 5 \Omega$  and if  $X_L$  at resonance is 300 Ω, the bandwidth is \_\_\_\_\_.
- [a] 200 Hz      [b] 60 Hz      [c] 40 Hz      [d] 8 Hz
17. You have to connect 1500 Ω resistor in a circuit but you have some 1000 Ω resistors only, how would you connect 1000 Ω resistors to obtain 1500 Ω?
- [a] 2 in parallel      [b] 2 in parallel and 1 in series      [c] 2 in series      [d] 2 in series and 1 in parallel
18. In a resonant circuit, the resonant frequency bisects the bandwidth if quality factor (Q) is \_\_\_\_\_.
- [a] less than 10      [b] not equal to 10      [c] greater than or equal to 10      [d] equal to 0
19. If the load has a capacitive reactance,
- [a] then  $\theta$  is positive and the current lags voltage  
 [b] then  $\theta$  is negative and the current lags voltage  
 [c] then  $\theta$  is positive and the current leads voltage  
 [d] then  $\theta$  is negative and the current leads voltage
20. Which of the following statement is correct for the balanced three phase star connected system
- [a]  $V_L = V_\phi$  and  $I_\phi = I_L$       [b]  $V_L = \sqrt{3}V_\phi$  and  $I_\phi = I_L$   
 [c]  $V_L = V_\phi$  and  $\sqrt{3}I_\phi = I_L$       [d]  $V_L = V_\phi$  and  $I_\phi = \sqrt{3}I_L$